



Note: R2 seems wasteful. But consider that it will only source current into the zener when the sun is out and energy is regenerated into the batteries, because when there is no sun, the sensor voltage will be well below 1V, so the "waste" is well compensated and it gives a better bias and more reliable filtering of spikes.